

Name : Siddharth Sanskritayan
Roll No. : 1901CS75

classmate
Date _____
Page _____

CS 226 - Lab 8

Q1) Control bits : (4x1 MUX used)

I_0	I_1	Function
0	0	Stop counting
0	1	Count up by 1
1	0	Count down by 1
1	1	Count up by 2

i) SR flip flop:

a) Count up by 1:

Notations:

$P \rightarrow$ present state

$N \rightarrow$ next state

$\langle \text{sub} \rangle 1 \rightarrow$ MSB

$\langle \text{sub} \rangle 0 \rightarrow$ LSB

We use the excitation table for each flip flop:

	P_1	P_0	N_1	N_0	S_1	R_1	S_0	R_0
$0 \rightarrow 1$	0	0	0	1	0	X	1	0
$1 \rightarrow 2$	0	1	1	0	1	0	0	1
$2 \rightarrow 3$	1	0	1	1	X	0	1	0
$3 \rightarrow 0$	1	1	0	0	0	1	0	1

Using K-map for S_1, R_1, S_0 and R_0 , we get

$$S_1 = \overline{P_1} \overline{P_0}$$

$$R_1 = \overline{P_1} P_0$$

$$S_0 = \overline{P_0}$$

$$R_0 = P_0$$

P_1	P_0	S_1	R_1
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

b) Count down by 1:

P_1	P_0	N_1	N_0	S_1	R_1	S_0	R_0
0	0	1	1	1	0	1	0
0	1	0	0	0	X	0	1
1	0	0	1	0	1	1	0
1	1	1	0	X	0	0	1

$$S_1 = \overline{P_1} \overline{P_0} \quad R_1 = P_1 \overline{P_0}$$

$$S_0 = \overline{P_0} \quad R_0 = P_0$$

c) Count up by 2:

P_1	P_0	N_1	N_0	S_1	R_1	S_0	R_0
0	0	1	0	1	0	0	X
0	1	1	1	1	0	X	0
1	0	0	0	0	1	0	X
1	1	0	1	0	1	X	0

$$S_1 = \overline{P_1} \quad R_1 = P_1$$

$$S_0 = 0 \quad R_0 = 0$$

ii) JK Flip flop :

a) Count up by 1 :

P_1	P_0	N_1	N_0	J_1	K_1	J_0	K_0
0	0	0	1	0	X	1	X
0	1	1	0	1	X	X	1
1	0	1	1	X	0	1	X
1	1	0	0	X	1	X	1

$$J_1 = P_0$$

$$K_1 = P_0$$

$$J_0 = 1$$

$$K_0 = 1$$

b) Count down by 1 :

P_1	P_0	N_1	N_0	J_1	K_1	J_0	K_0
0	0	1	1	1	X	1	X
0	1	0	0	0	X	X	1
1	0	0	1	X	1	1	X
1	1	1	0	X	0	X	1

$$J_1 = \overline{P_0}$$

$$K_1 = \overline{P_0}$$

$$J_0 = 1$$

$$K_0 = 1$$

c) Count up by 2 :

P_1	P_0	N_1	N_0	J_1	K_1	J_0	K_0
0	0	1	0	1	X	0	X
0	1	1	1	1	X	X	0
1	0	0	0	X	1	0	X
1	1	0	1	X	1	X	0

$$J_1 = 1$$

$$K_1 = 1$$

$$J_0 = 0$$

$$K_0 = 0$$

iii) Using T and D flip flops:
(shown in the same table)

a) Count up by 1 :

P_1	P_0	N_1	N_0	T_1	T_0	D_1	D_0
0	0	0	1	0	1	0	1
0	1	1	0	1	1	1	0
1	0	1	1	0	1	1	1
1	1	0	0	1	1	0	0

For D flip flop :

$$D_1 = P_1 \bar{P}_0 + P_0 \bar{P}_1 = P_1 \oplus P_0$$

$$D_0 = \bar{P}_0$$

For T flip flop :

$$T_1 = P_0$$

$$T_0 = 1$$

b) Count down by 1:

P_1	P_0	N_1	N_0	T_1	T_0	D_1	D_0
0	0	1	1	1	1	1	1
0	1	0	0	0	1	0	0
1	0	0	1	1	1	0	1
1	1	1	0	0	1	1	0

$$\left. \begin{array}{l} T_1 = \overline{P_1} \\ T_0 = 1 \end{array} \right\} \text{for T flip flop}$$

$$\left. \begin{array}{l} D_1 = P_1 P_0 + \overline{P_1} \overline{P_0} = P_1 \text{ XOR } P_0 \\ D_0 = \overline{P_0} \end{array} \right\} \text{for D flip flop}$$

c) Count up by 2:


P_1	P_0	N_1	N_0	T_1	T_0	D_1	D_0
0	0	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	0
1	1	0	1	1	0	1	0

for D flip flop:


$$D_1 = \overline{P_1} \quad D_0 = P_0$$

for T flip flop:


$$T_1 = 1 \quad T_0 = 0$$

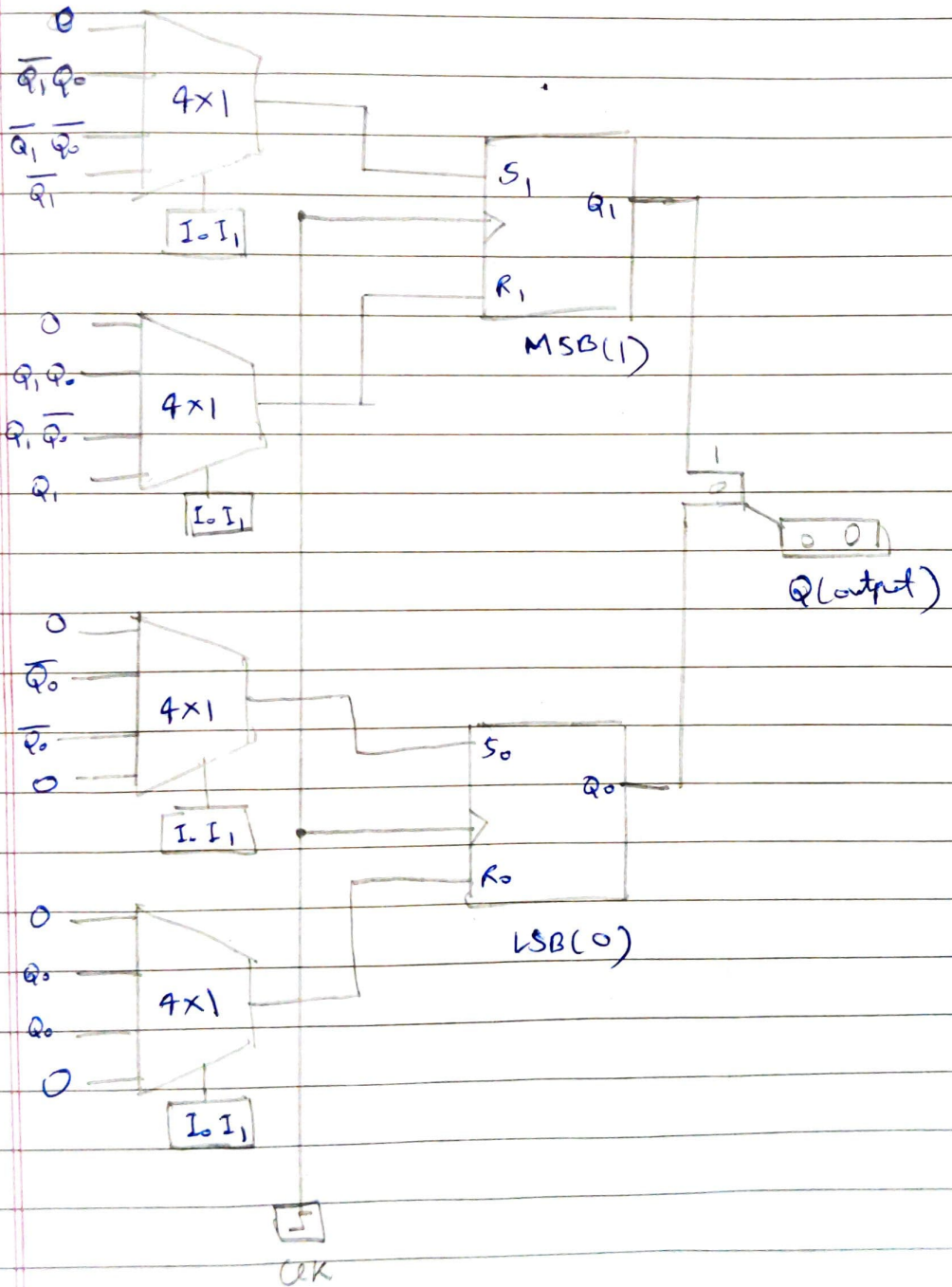Designs :i) SR Flip Flop :

ii) J K Flip Flop :

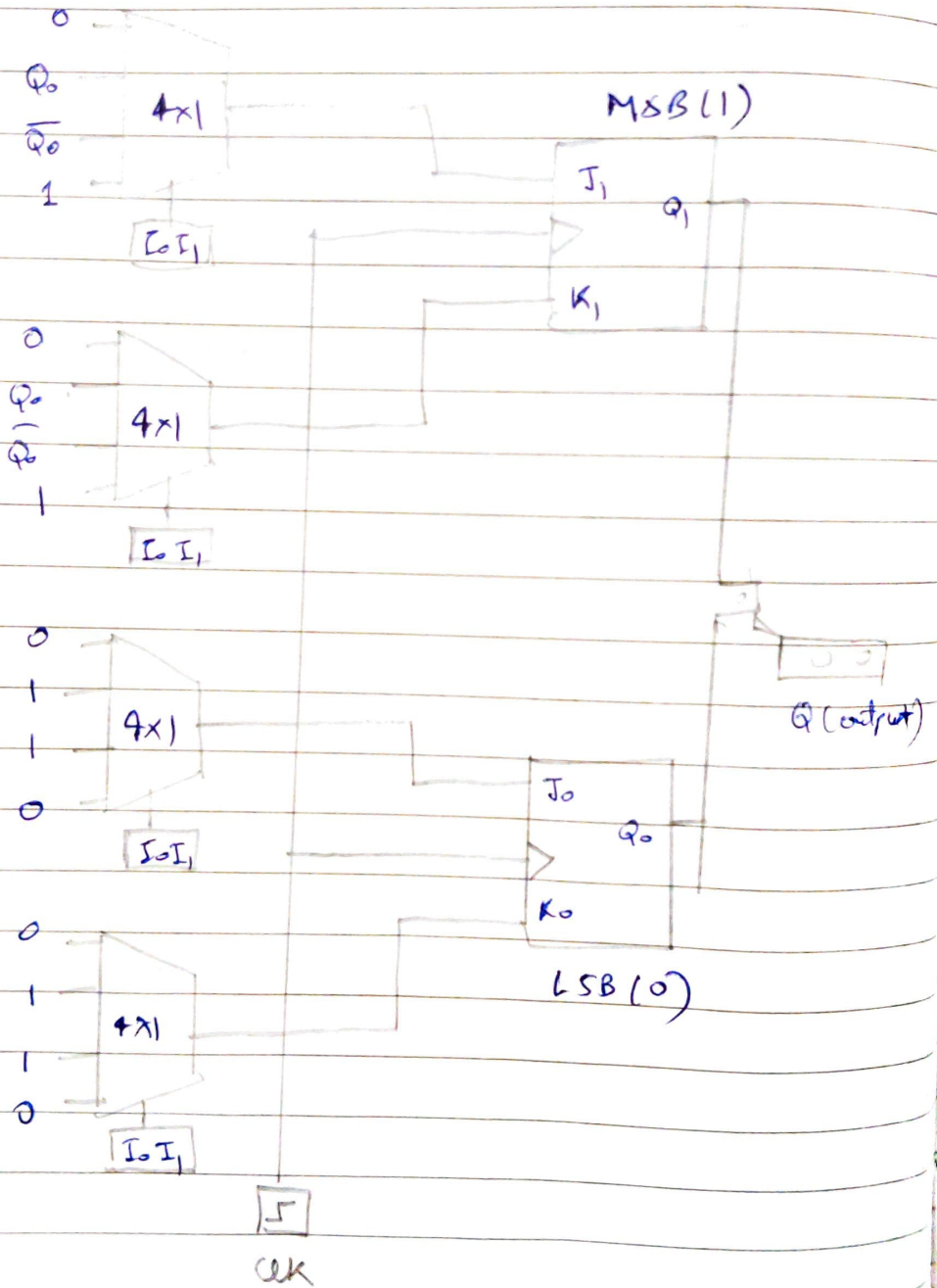

iii) T Flip Flop :

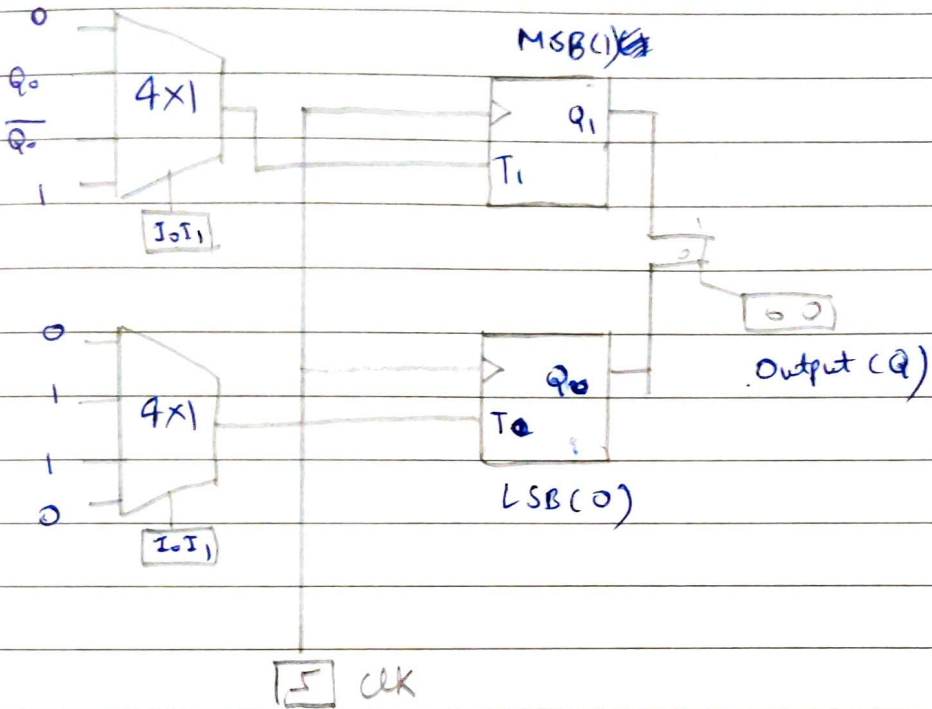

iv) D Flip Flop :

